



Verilog-HDL 기반 4bit binary Adder 설계

Shinwoong Kim

Hardware Description Language (HDL)

- Manual method for designing logic circuits **are feasible only** when the **circuit is small**
- Practically, designers use computer-based design tools
 - ✓ All modern design tools rely on a hardware description language(HDL) to describe the circuit
 - ✓ It is like C, C++, Java or Python (programming language)
- The most widely used language is **Verilog** and **VHDL**
 - ✓ They have many similarities
 - ✓ Verilog-HDL is the more common in industry
 - It is an easier than VHDL to describe, learn and use

Half-Adder

```

module Half_Adder ( x, y, C, S );
    input x, y;
    output C, S;

    //Continuous assignment type
    assign S = x^y; // XOR
    assign C = x&y; // AND

endmodule

```

**port list*

**port declaration*

**Body*

**Comment*



```

module Half_Adder ( x, y, C, S );

input x, y;
output C, S;
reg C, S;


//Procedure assignment type
always@(x or y) begin // same as "always@(*) begin"
    S = x^y;
    C = x&y;
end

endmodule


```

Half Adder

<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Full-Adder

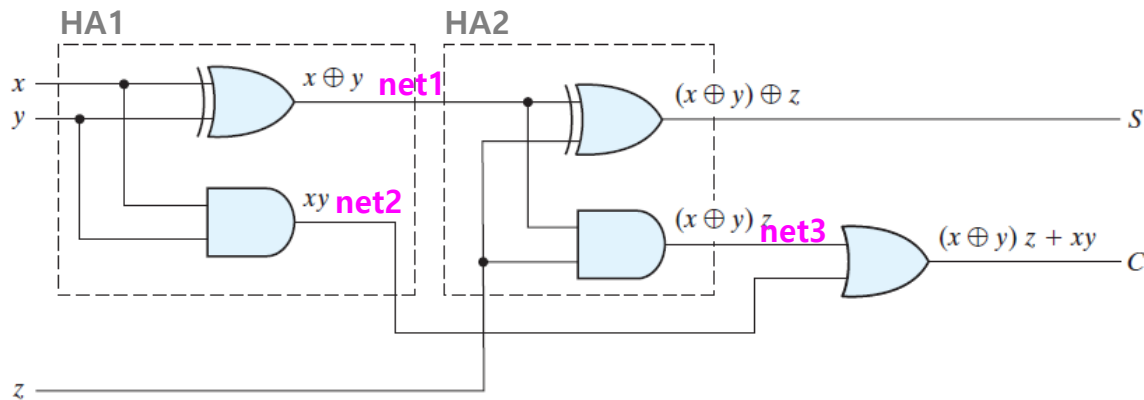

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

```

module Full_Adder ( x, y, z, C, S );

input x, y, z;
output C, S;

wire net1, net2, net3;


    //Continuous assignment type
    //for HA1
    assign net1 = x^y; // XOR
    assign net2 = x&y; // AND

    //for HA2
    assign S = net1^z; // XOR
    assign net3 = net1&z; // AND

    //for C
    assign C = net3 | net2; // OR

endmodule
    
```

Binary 4-bit Adder

 

```

module Binary_4bit_Adder ( A, B, C, Y );

input [3:0] A, B;
output C;
output [3:0] Y;

wire C1, C2, C3;

Full_Adder U0 ( .x(A[0]), .y(B[0]), .z(1'b0), .C(C1), .S(Y[0]) );
Full_Adder U1 ( .x(A[1]), .y(B[1]), .z(C1), .C(C2), .S(Y[1]) );
Full_Adder U2 ( .x(A[2]), .y(B[2]), .z(C2), .C(C3), .S(Y[2]) );
Full_Adder U3 ( .x(A[3]), .y(B[3]), .z(C3), .C(C), .S(Y[3]) );

endmodule
    
```

*Module Instantiation
(using Full_Adder
module)

Simulation: Binary 4-bit Adder

- Usually make 'test-bench' file first


*Environment to verify the design source

- ✓ Including an input condition

```
module tb_Binary_4bit_Adder();  
  
  reg [3:0] A_in, B_in;  
  wire C_out;  
  wire [3:0] Y_out;  
  
  Binary_4bit_Adder DUT(  
    .A(A_in),  
    .B(B_in),  
    .C(C_out),  
    .Y(Y_out)  
  );  
  
  initial begin  
    A_in = 4'b0011;  
    B_in = 4'b0110;  
  end  
  
endmodule
```


```
module Binary_4bit_Adder ( A, B, C, Y );  
  
  input [3:0] A, B;  
  output C;  
  output [3:0] Y;  
  
  wire C1, C2, C3;  
  
  Full_Adder U0 ( .x(A[0]), .y(B[0]), .z(1'b0), .C(C1), .S(Y[0]) );  
  Full_Adder U1 ( .x(A[1]), .y(B[1]), .z(C1), .C(C2), .S(Y[1]) );  
  Full_Adder U2 ( .x(A[2]), .y(B[2]), .z(C2), .C(C3), .S(Y[2]) );  
  Full_Adder U3 ( .x(A[3]), .y(B[3]), .z(C3), .C(C), .S(Y[3]) );  
  
endmodule
```

tb_Binary_4bit_Adder.v

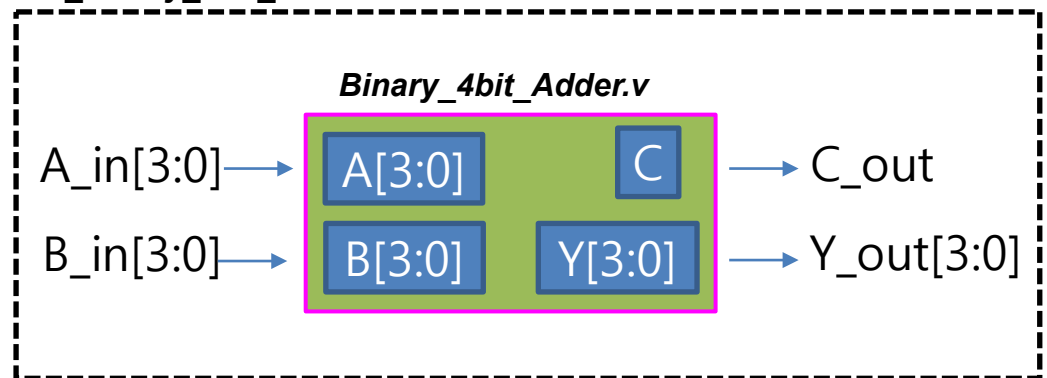

Simulation: Binary 4-bit Adder

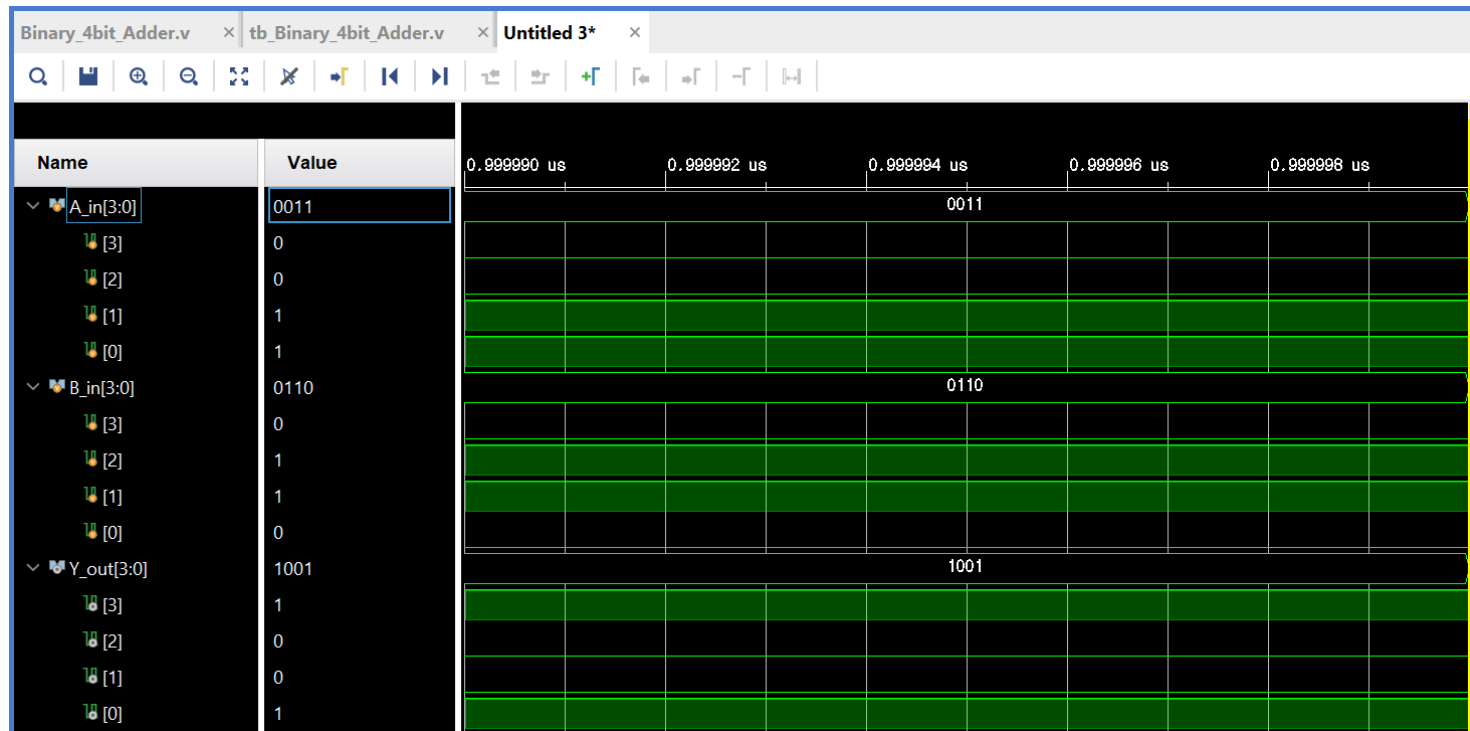- Simulation is also performed based on the computer-based tools
 - ✓ 1) Source code design
 - ✓ 2) Simulate it to verify the logic function



실험

- **Xilinx Vivado 프로그램에서 4bit binary adder 설계**
 - ✓ Full_Adder.v 작성
 - ✓ Binary_4bit_Adder.v 작성
- **Xilinx Vivado 프로그램에서 Simulation 수행**
 - ✓ 테스트 벤치 파일: tb_Binary_4bit_Adder.v 작성
 - 입력 A[3:0]: 4'b0011;
 - 입력 B[3:0]: 4'b0110;
 - ✓ 시뮬레이션 수행 → 조교 검사 후 퇴실 가능
- **[참고]**
 - ✓ 다음 주 실험은 금일 설계한 4bit adder + 7 segment display decoder를 포함하여 실제 FPGA 보드에 실행해보는 작업 수행 예정
 - 따라서, 설계 data를 잘 간직하기 바람