



Logic Gates

Shinwoong Kim

Binary Logic

- **Binary logic**


- ✓ Binary logic consists of **binary variables** and a set of **logical operations**

- **Two values as the variables**


- ✓ True and false, yes or no, etc.
- ✓ In terms of binary bits, '0' and '1' → e.g., 0V and 5V

- **Logical operation**

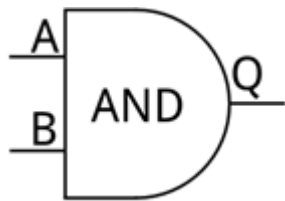- ✓ Three basic logical operation: AND, OR, NOT



Q is '1' when A='1' and B='1'
Otherwise, Q is '0'

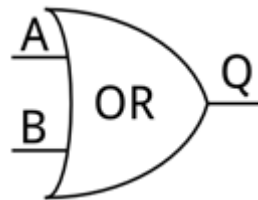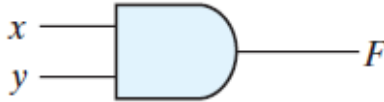

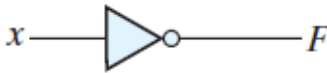



Q is '1' when A='1' or B='1'
Otherwise, Q is '0'







Complement operation
So, output is not A

Basic Logic Gates

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	





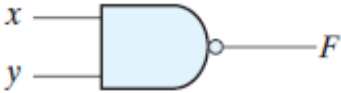
Basic Logic Gates

Name	Graphic symbol	Algebraic function	Truth table															
NAND		$F = (xy)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

Integrated Circuit

- IC

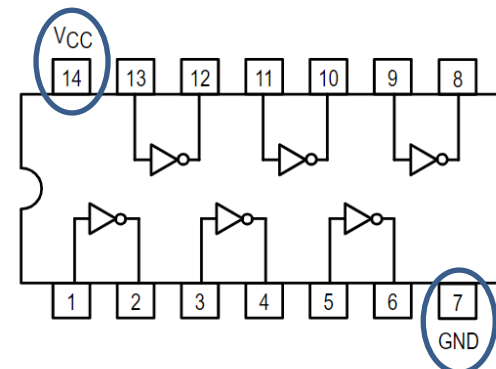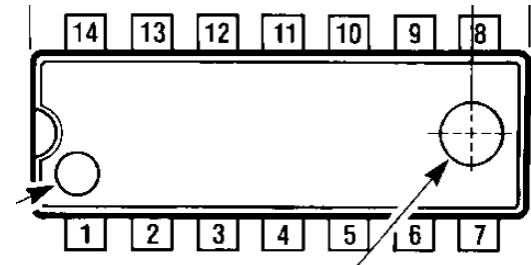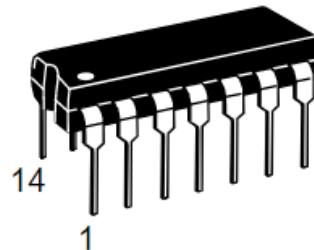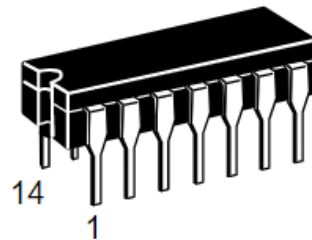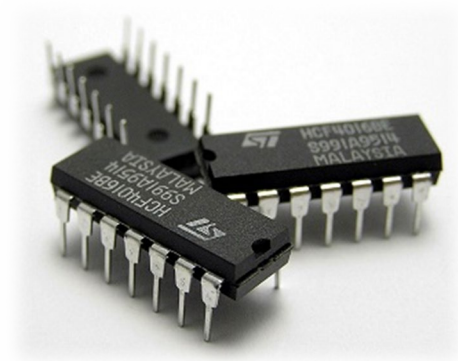- ✓ is a set of electronic circuits on one small flat piece (or "chip") of semiconductor material, usually silicon
- ✓ For example, **Inverter (7404)** gates
 - Power (VCC), Ground (GND), input pins, output pins



Integrated Circuit

- Datasheet

- ✓ 각 칩에 대해서 자세한 설명을 해 놓은 자료
- ✓ 제품명만 검색해도 많은 datasheet가 검색 됨

FAIRCHILD
SEMICONDUCTOR™

August 1986
Revised March 2000

DM74LS04 Hex Inverting Gates

General Description


This device contains six independent gates each of which performs the logic INVERT function.

Ordering Code:

Order Number	Package Number	Package Description
DM74LS04M	M14A	14-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-120, 0.150 Narrow
DM74LS04SJ	M14D	14-Lead Small Outline Package (SOP), EIAJ TYPE II, 5.3mm Wide
DM74LS04N	N14A	14-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300 Wide

Devices also available in Tape and Reel. Specify by appending the suffix letter "X" to the ordering code.

Connection Diagram

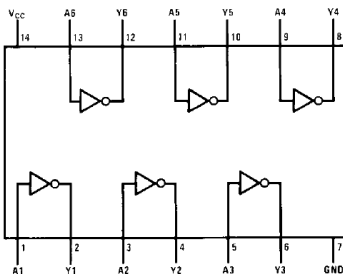

Function Table

$$Y = \bar{A}$$

Input	Output
A	Y
L	H
H	L

H = HIGH Logic Level
L = LOW Logic Level

DM74LS04 Hex Inverting Gates

Recommended Operating Conditions

Symbol	Parameter	Min	Nom	Max	Units
V _{CC}	Supply Voltage	4.75	5	5.25	V
V _{IH}	HIGH Level Input Voltage	2			V
V _{IL}	LOW Level Input Voltage			0.8	V
I _{OH}	HIGH Level Output Current			-0.4	mA
I _{OL}	LOW Level Output Current			8	mA
T _A	Free Air Operating Temperature	0		70	°C

Electrical Characteristics


over recommended operating free air temperature range (unless otherwise noted)

Symbol	Parameter	Conditions	Min	Typ (Note 2)	Max	Units
V _I	Input Clamp Voltage	V _{CC} = Min, I _I = -18 mA			-1.5	V
V _{OH}	HIGH Level Output Voltage	V _{CC} = Min, I _{OH} = Max, V _{IL} = Max	2.7	3.4		V
V _{OL}	LOW Level Output Voltage	V _{CC} = Min, I _{OL} = Max, V _{IH} = Min		0.35	0.5	V
I _I	Input Current @ Max Input Voltage	I _{OL} = 4 mA, V _{CC} = Min, V _{CC} = Max, V _I = 7V		0.25	0.4	mA
I _{IH}	HIGH Level Input Current	V _{CC} = Max, V _I = 2.7V			20	μA
I _{IL}	LOW Level Input Current	V _{CC} = Max, V _I = 0.4V			-0.36	mA
I _{OS}	Short Circuit Output Current	V _{CC} = Max (Note 3)	-20		-100	mA
I _{COH}	Supply Current with Outputs HIGH	V _{CC} = Max		1.2	2.4	mA
I _{CCL}	Supply Current with Outputs LOW	V _{CC} = Max		3.6	6.6	mA


Note 2: All measurements at V_{CC} = 5V, T_A = 25°C.

Integrated Circuit


7400

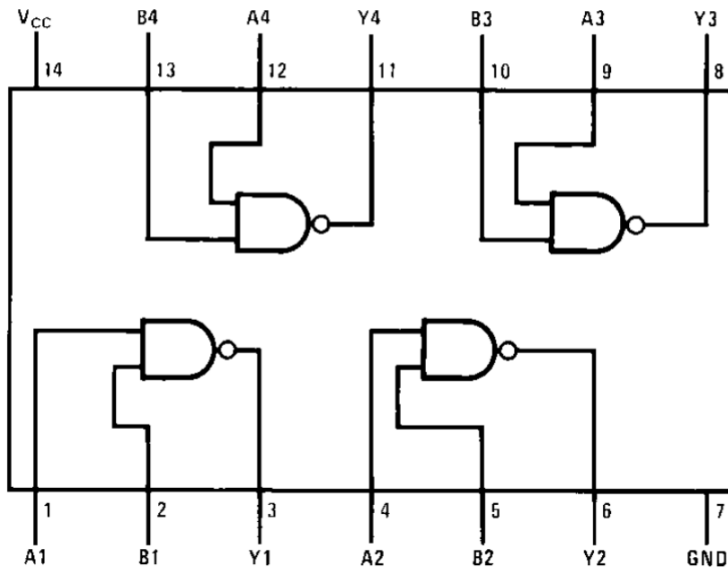


7402

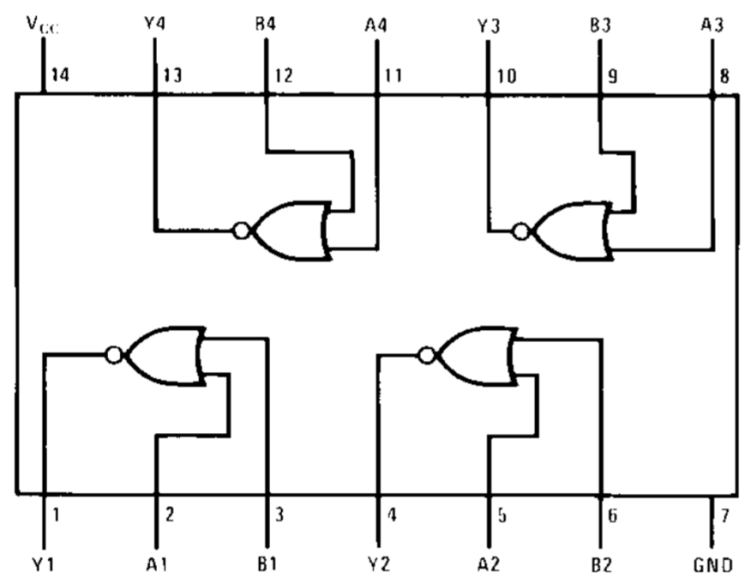

7408

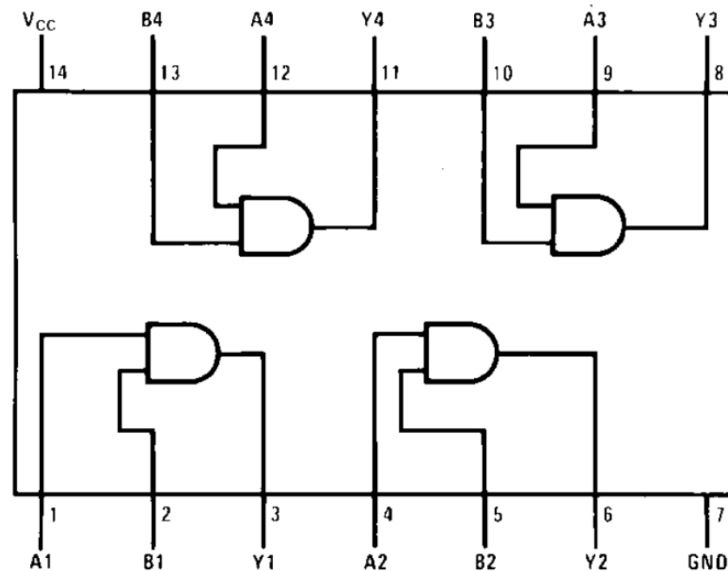


7432

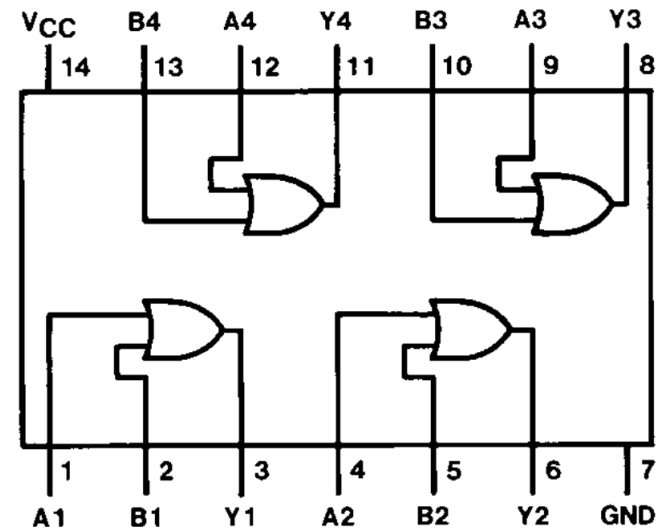


Integrated Circuit

- IC type

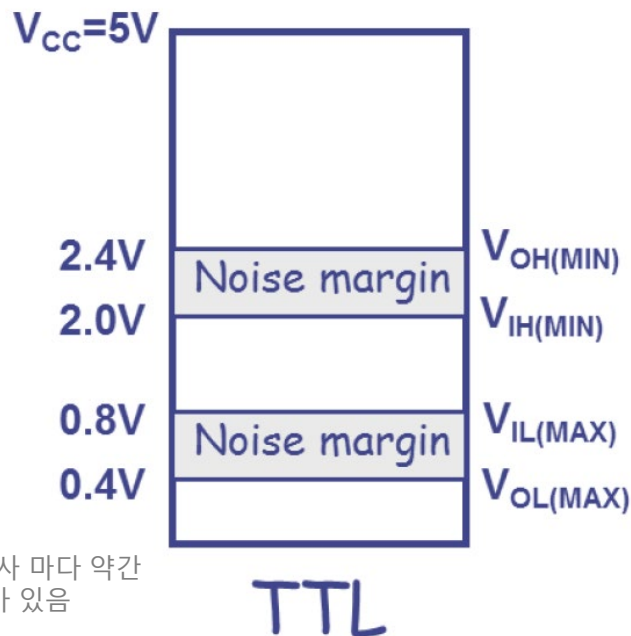- ✓ TTL(transistor-transistor logic)
 - 74LS00, 74LS02 ... (low power shorttky TTL)
- ✓ CMOS (Complementary metal-oxide semiconductor)
 - 74HC00, 74HC02 ... (high speed CMOS)





*제조사 마다 약간
차이가 있음

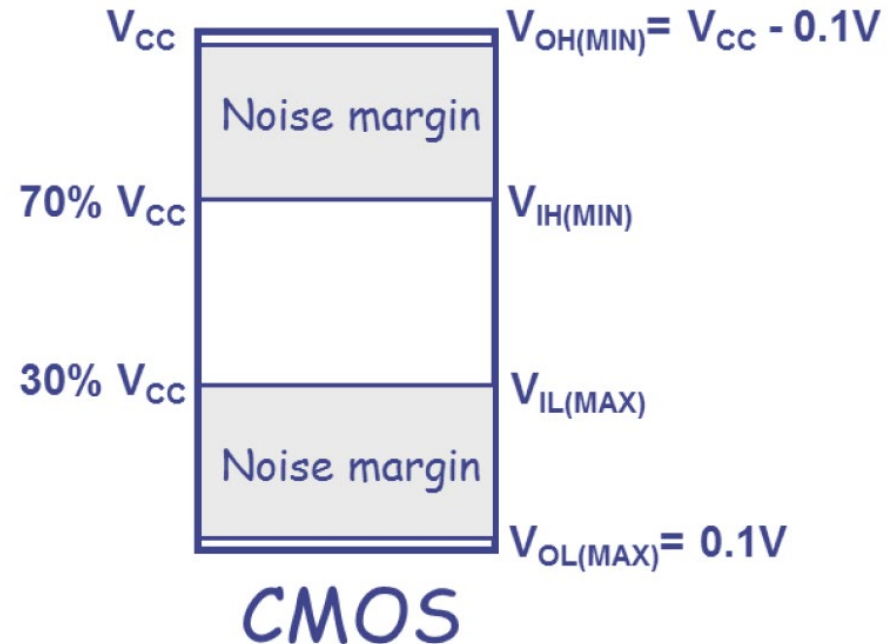

Characteristic: Noise margin

- Noise margin

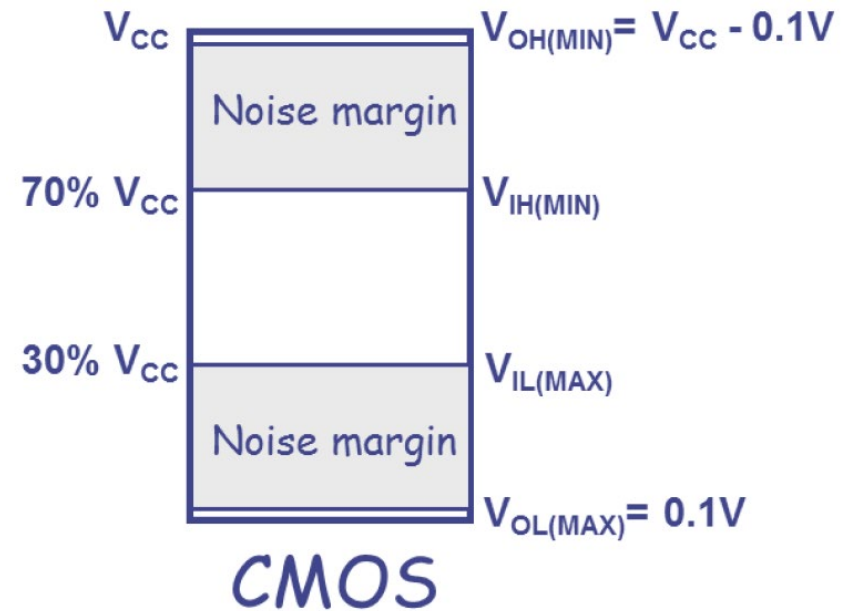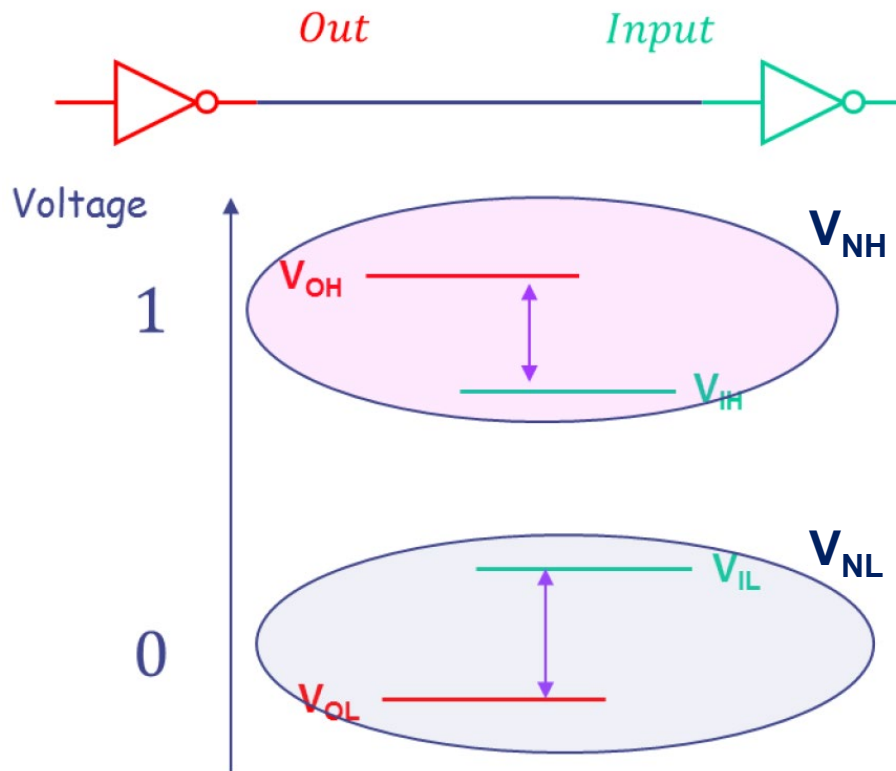- $V_{NH} = V_{OH(min)} - V_{IH(min)}$
- $V_{NL} = V_{IL(max)} - V_{OL(max)}$



Characteristic: Noise margin

- **Issue**

CMOS --> TTL


Sending Low (**0.1V** -> **0.8V**)

Sending High (**4.9V** -> **2.0V**)

TTL --> CMOS


Sending Low (**0.4V** -> **1.5V**) Pass

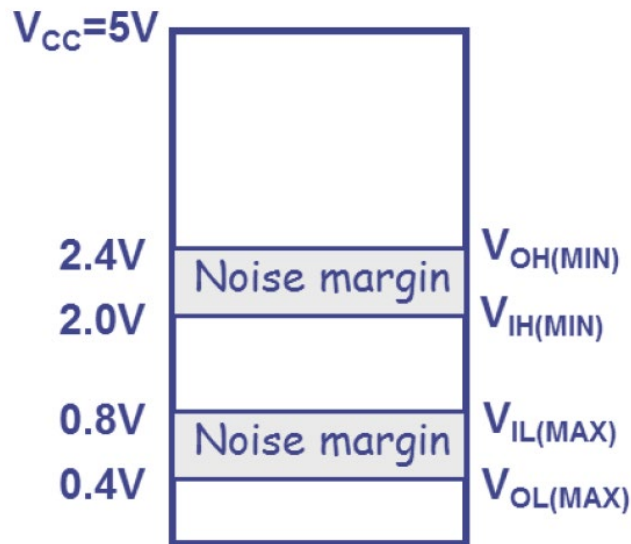Sending High (**2.4V** -> **3.5V**) No Pass!



*제조사 마다 약간 차이가 있음

TTL

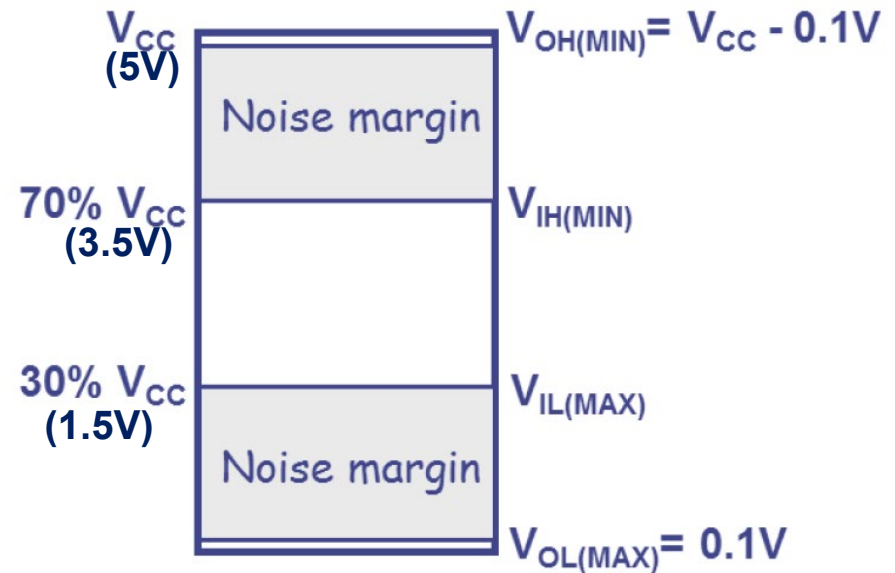

CMOS

Characteristic: Noise margin

- e.g., Datasheet (74LS04)

Recommended Operating Conditions

Symbol	Parameter	Min	Nom	Max	Units
V_{CC}	Supply Voltage	4.75	5	5.25	V
V_{IH}	HIGH Level Input Voltage	2			V
V_{IL}	LOW Level Input Voltage			0.8	V
I_{OH}	HIGH Level Output Current			-0.4	mA
I_{OL}	LOW Level Output Current			8	mA
T_A	Free Air Operating Temperature	0		70	°C

Electrical Characteristics

over recommended operating free air temperature range (unless otherwise noted)

Symbol	Parameter	Conditions	Min	Typ (Note 2)	Max	Units
V_I	Input Clamp Voltage	$V_{CC} = \text{Min}, I_I = -18 \text{ mA}$			-1.5	V
V_{OH}	HIGH Level Output Voltage	$V_{CC} = \text{Min}, I_{OH} = \text{Max}, V_{IL} = \text{Max}$	2.7	3.4		V
V_{OL}	LOW Level Output Voltage	$V_{CC} = \text{Min}, I_{OL} = \text{Max}, V_{IH} = \text{Min}$		0.35	0.5	V
		$I_{OL} = 4 \text{ mA}, V_{CC} = \text{Min}$		0.25	0.4	
I_I	Input Current @ Max Input Voltage	$V_{CC} = \text{Max}, V_I = 7V$			0.1	mA
I_{IH}	HIGH Level Input Current	$V_{CC} = \text{Max}, V_I = 2.7V$			20	μA
I_{IL}	LOW Level Input Current	$V_{CC} = \text{Max}, V_I = 0.4V$			-0.36	mA
I_{OS}	Short Circuit Output Current	$V_{CC} = \text{Max}$ (Note 3)	-20		-100	mA
I_{CCH}	Supply Current with Outputs HIGH	$V_{CC} = \text{Max}$		1.2	2.4	mA
I_{CCL}	Supply Current with Outputs LOW	$V_{CC} = \text{Max}$		3.6	6.6	mA

Characteristic: Noise margin

- e.g., Datasheet (74HC04)

Type 74HC04

At recommended operating conditions; voltages are referenced to GND (ground = 0 V).

SYMBOL	PARAMETER	TEST CONDITIONS		MIN.	TYP.	MAX.	UNIT
		OTHER	V _{CC} (V)				
T _{amb} = 25 °C							
V _{IH}	HIGH-level input voltage		2.0	1.5	1.2	–	V
			4.5	3.15	2.4	–	V
			6.0	4.2	3.2	–	V
V _{IL}	LOW-level input voltage		2.0	–	0.8	0.5	V
			4.5	–	2.1	1.35	V
			6.0	–	2.8	1.8	V
V _{OH}	HIGH-level output voltage	V _I = V _{IH} or V _{IL}					
		I _O = –20 μA	2.0	1.9	2.0	–	V
		I _O = –20 μA	4.5	4.4	4.5	–	V
		I _O = –4.0 mA	4.5	3.98	4.32	–	V
		I _O = –20 μA	6.0	5.9	6.0	–	V
		I _O = –5.2 mA	6.0	5.48	5.81	–	V
V _{OL}	LOW-level output voltage	V _I = V _{IH} or V _{IL}					
		I _O = 20 μA	2.0	–	0	0.1	V
		I _O = 20 μA	4.5	–	0	0.1	V
		I _O = 4.0 mA	4.5	–	0.15	0.26	V
		I _O = 20 μA	6.0	–	0	0.1	V
		I _O = 5.2 mA	6.0	–	0.16	0.26	V
I _{IL}	input leakage current	V _I = V _{IH} or V _{IL}	6.0	–	0.1	±0.1	μA

Characteristic: Delay


- **Transition time**

- ✓ Transition High-to-Low (t_{THL})

- 출력이 high 90% → low 10%가 될 때까지의 시간

- ✓ Transition Low-to-High (t_{TLH})

- 출력이 low 10% → high 90%가 될 때까지의 시간

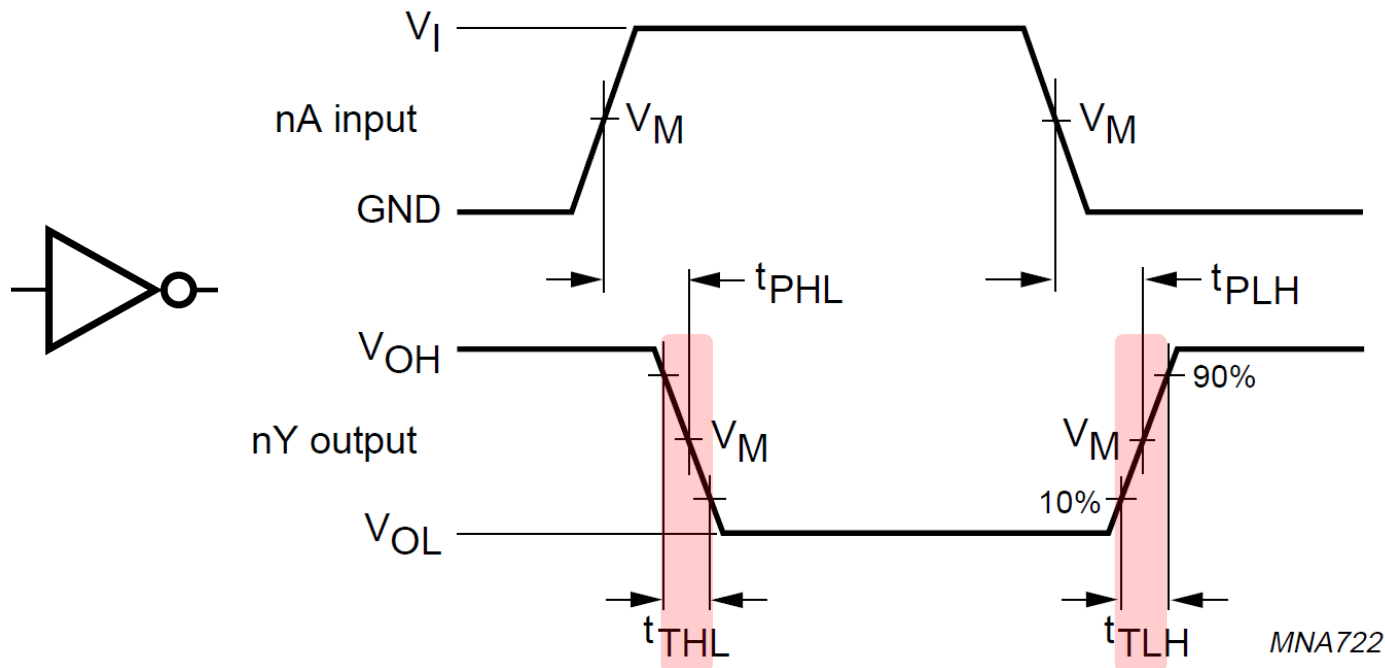

Characteristic: Delay


- Propagation time

- ✓ Propagation High-to-Low (t_{PHL})

- 출력이 High \rightarrow Low가 될 때, 입력 신호와의 시간 차이
(50% 지점 간의 차이)

- ✓ Propagation Low-to-High (t_{PLH})



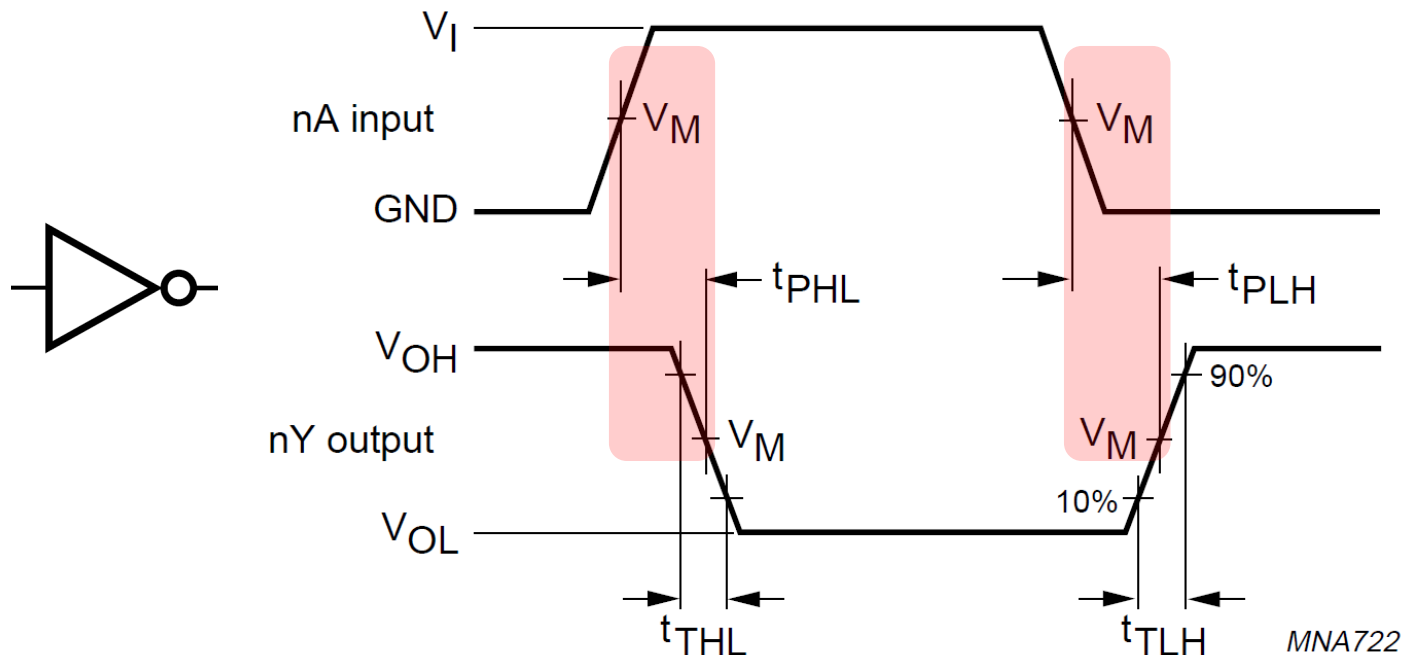
- 출력이 Low \rightarrow High가 될 때, 입력 신호와의 시간 차이
(50% 지점 간의 차이)



Light-Emitting Diode (LED)

• 동작

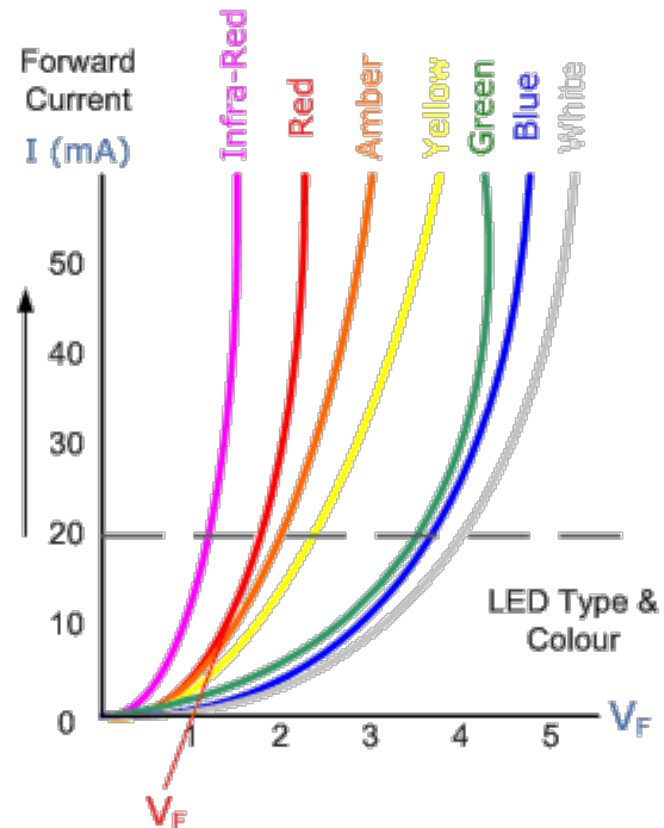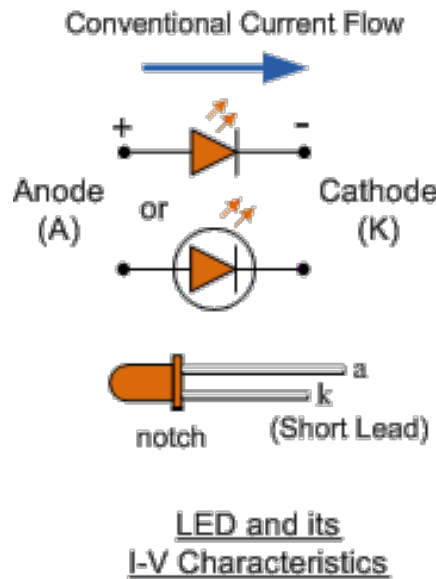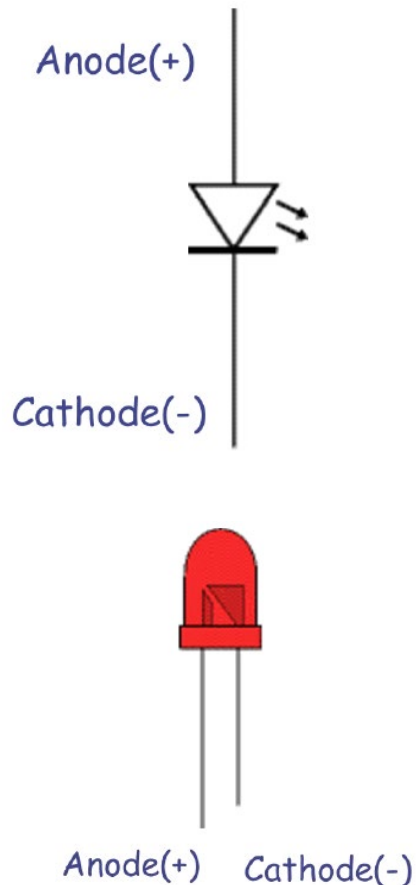- ✓ Anode(+) 전압 > Cathode(-) 전압인 경우, 즉 순방향으로 전압을 가했을 경우, 전류가 흐르며 발광(發光)함, 밝기는 전류에 비례함




*https://www.electronics-tutorials.ws/diode/diode_8.html

Light-Emitting Diode (LED)

• 회로 구성

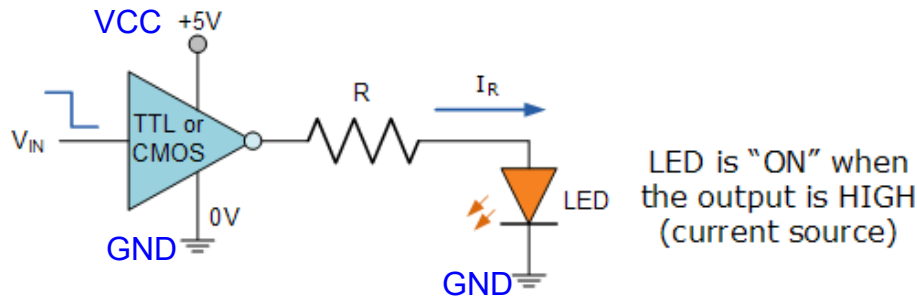
- ✓ 전류 제한을 위해 저항과 함께 사용
 - LED는 일반적으로 $V_F=2V$ 에서 20mA 정도 소모
- ✓ 로직 출력이 'High(5V)'일 때 LED가 켜지도록 하는 경우



*필요한 저항 값 계산



$$R = \frac{5V - 2V}{20mA} = 150\Omega$$

- ✓ 로직 출력이 'Low(0V)'일 때 LED가 켜지도록 하는 경우

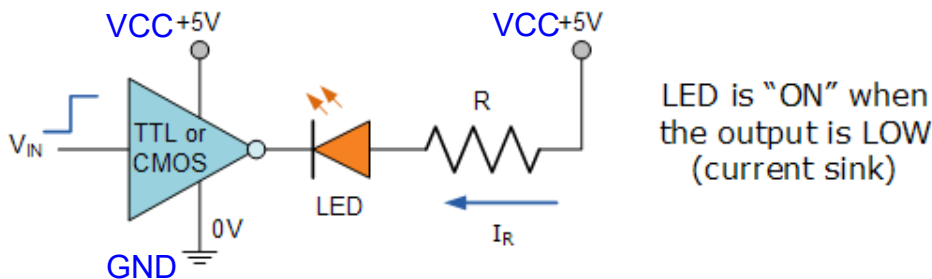



실험 1

• 기본 로직 동작 검증 (74LS00 NAND)

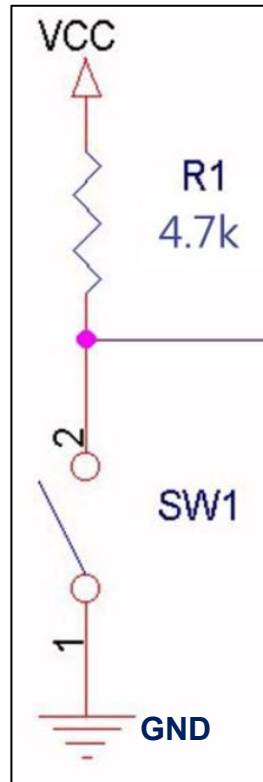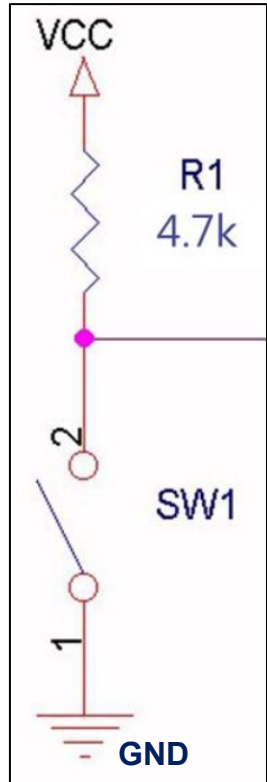

*Pull-up 저항을
이용한 입력 스위치

OFF: VCC 연결 (logic high)
ON: GND 연결 됨 (logic low)

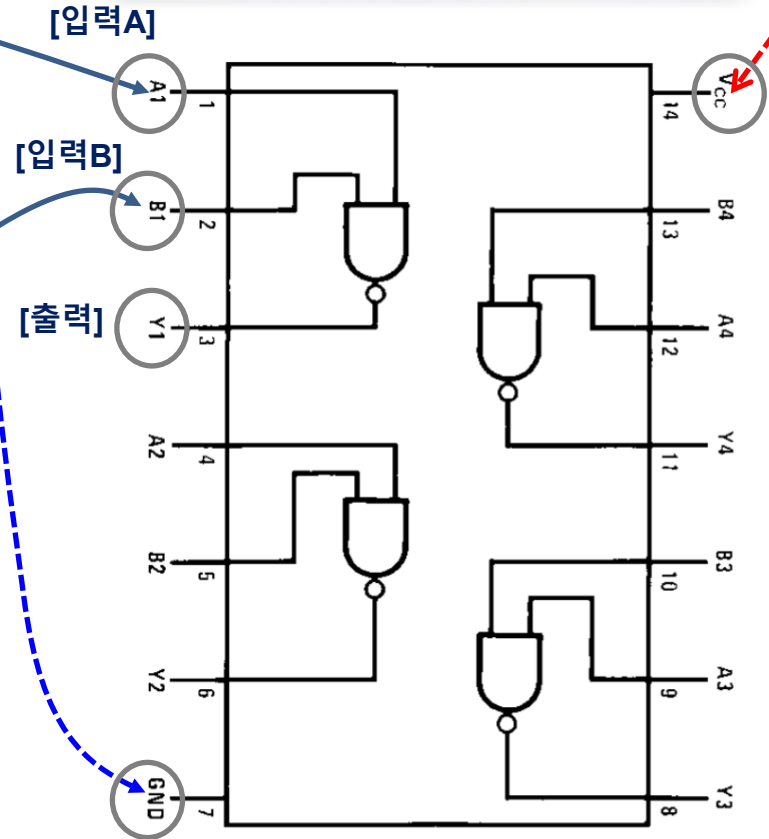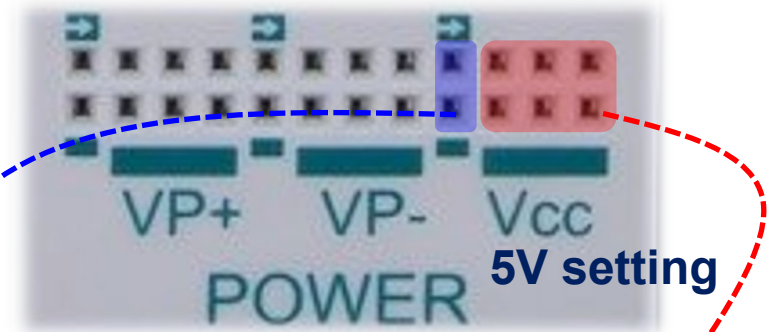

실험 1

- 기본 로직 동작 검증 (74LS00 NAND)

✓ DMM을 이용하여 출력 전압을 측정하고 → 출력 논리를 판별


74LS00
(NAND)

입력 논리		예상 출력 논리	측정된 출력 전압	측정된 전압으로부터 얻은 논리
A	B	0 or 1?	? V	0 or 1?
0	0			
0	1			
1	0			
1	1			

실험 2

• 인가하는 전압 범위에 따른 특성 파악

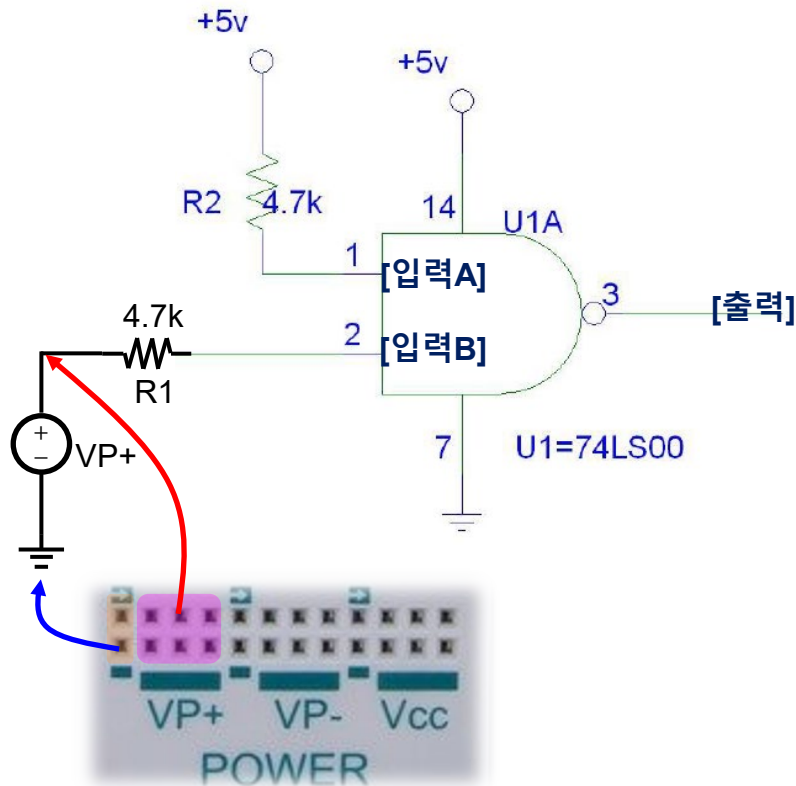- ✓ ‘실험1’에 이어서 진행, 입력 스위치 부분만 변경하면 됨
- ✓ 입력 A (1번 핀) : 4.7kΩ을 이용하여 논리 high (VCC 5V)에 고정
- ✓ 입력 B (2번 핀) : VP+ power에 연결하여 다양한 전압을 인가
- ✓ [참고] Datasheet 기준, 74LS00의 $V_{IL(max)}=0.8V$, $V_{IH(min)}=2.0V$




입력 전압 [입력 B]	예상 출력 논리	측정된 출력 전압	측정된 전압으로부터 얻은 논리
[V]	0 or 1?	? V	0 or 1?
0			
0.4			
0.8			
1.2			
1.6			
2.0			
3.0			
4.0			
5.0			

실험 3

• XOR 회로 설계

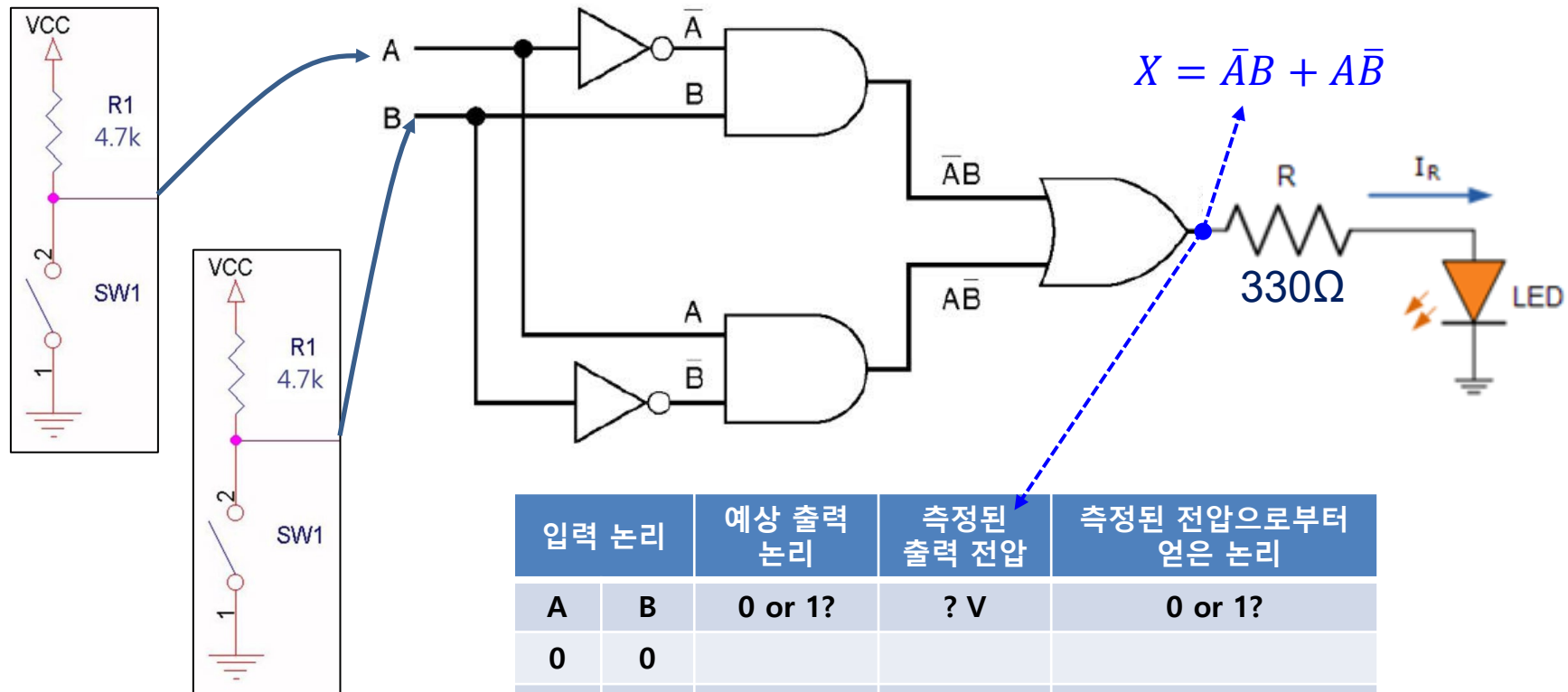- Inverter(74LS04) + AND(74LS08) + OR(74LS32) 사용
- LED 사용하여 출력 로직 판별 (출력이 'High'일 때 LED ON)






입력 논리		예상 출력 논리	측정된 출력 전압	측정된 전압으로부터 얻은 논리
A	B	0 or 1?	? V	0 or 1?
0	0			
0	1			
1	0			
1	1			

보드 구성 예

• 보드 구성

- ✓ 전원은 Vcc 사용 (5V)

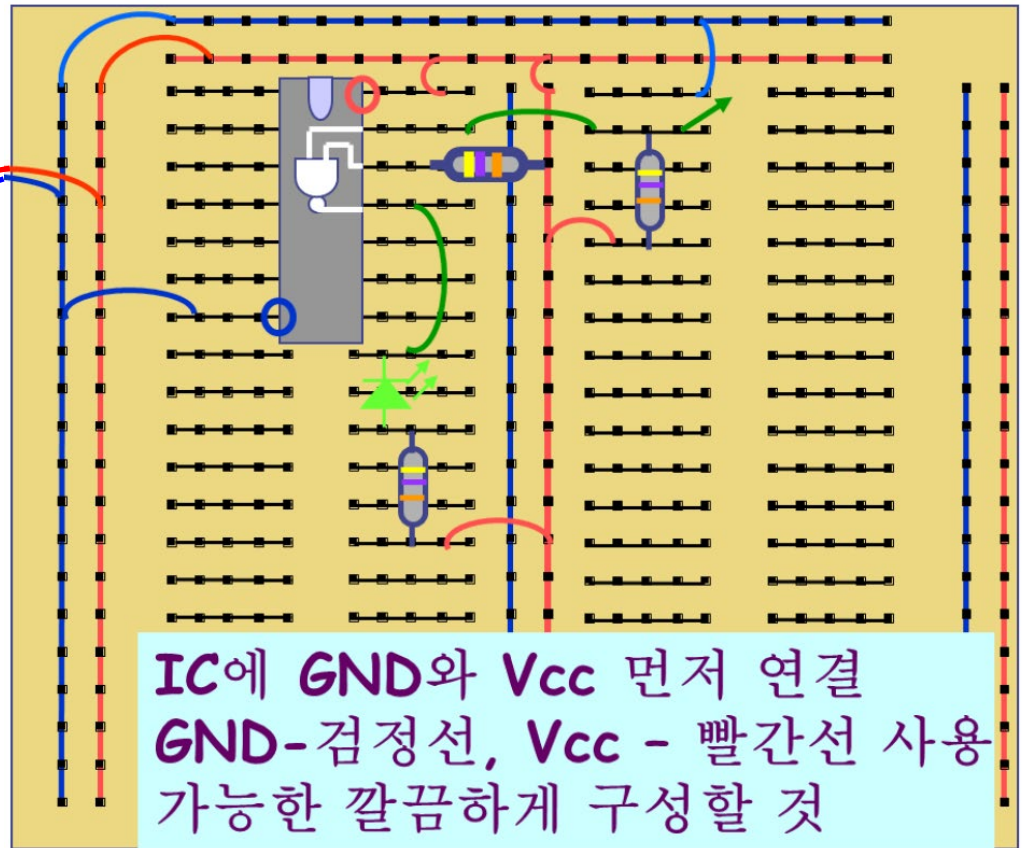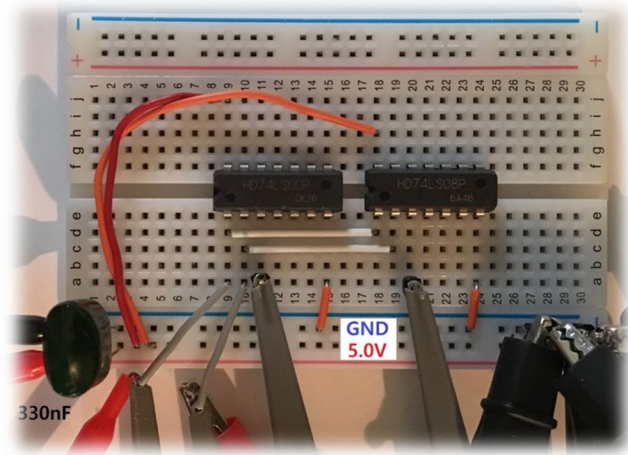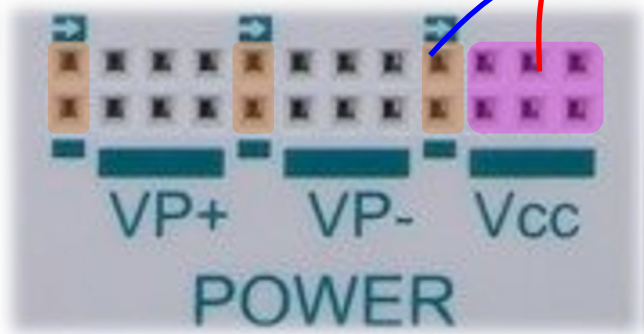

IC에 GND와 Vcc 먼저 연결
GND-검정선, Vcc - 빨간선 사용
가능한 깔끔하게 구성할 것

<https://m.blog.naver.com/PostView.naver?isHttpsRedirect=true&blogId=specialist0&logNo=221247815110>