




# 4bit binary Adder 구현 (FPGA 프로그래밍)

**Shinwoong Kim**

 
# Integrated Circuit (IC)

- **Small/medium-scale integration (SSI, MSI)**

- ✓ It contains only a few transistors → a few logic gates
- ✓ In case of small size system, it can be designed by the discrete logic gate IC
  - State diagram → state table → K-map → state equation → implement system



 \*[https://manual.eg.poly.edu/index.php/Introduction\\_to\\_Digital\\_Logic](https://manual.eg.poly.edu/index.php/Introduction_to_Digital_Logic)




\*<https://www.instructables.com/Digital-Combination-Lock/>

# FPGA

- **Field Programmable Gate Array**

- ✓ Consists of simple programmable logic blocks and massive fabric of interconnection

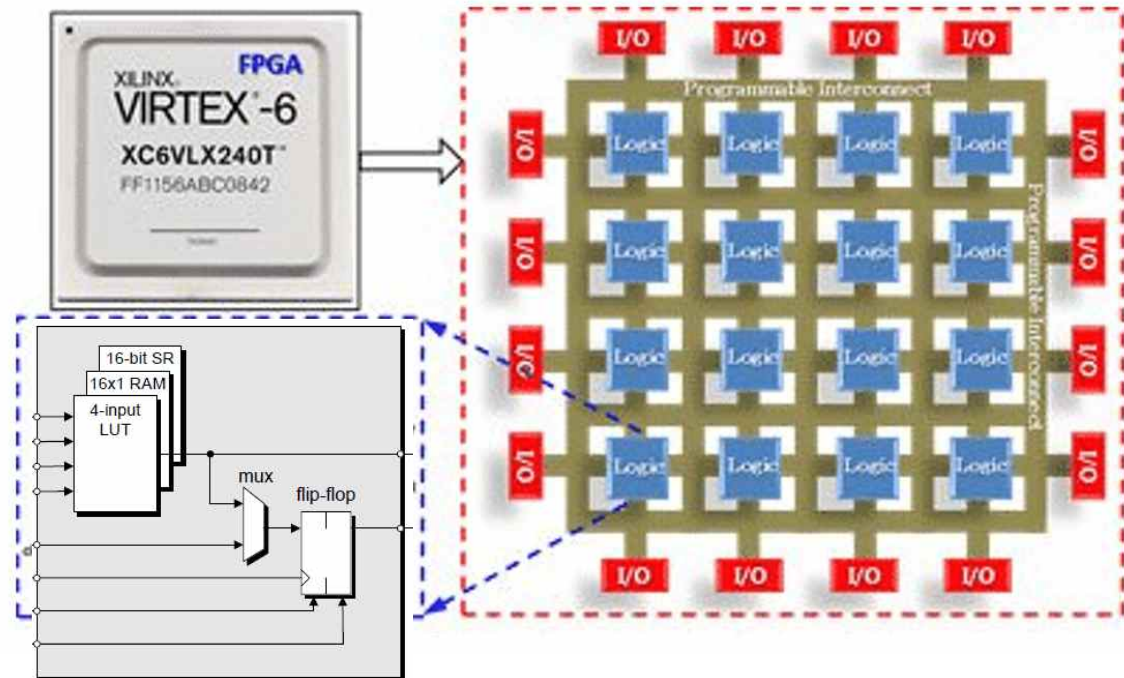\*[https://www.researchgate.net/figure/FPGA-architecture-description\\_fig3\\_308883347](https://www.researchgate.net/figure/FPGA-architecture-description_fig3_308883347)




- Large number of Logic blocks (LUT, MUX, FF)
- User programmable interconnection

# Circuit Compilation


- 1. Technology mapping

 - 1) Designed by Verilog-HDL
- 2) Logic synthesis (Verilog → logic gates) by SW



 
- 2. Placement

Assign a logical LUT to a physical location



 - 3. Routing



Select wire segments and Switches for interconnection




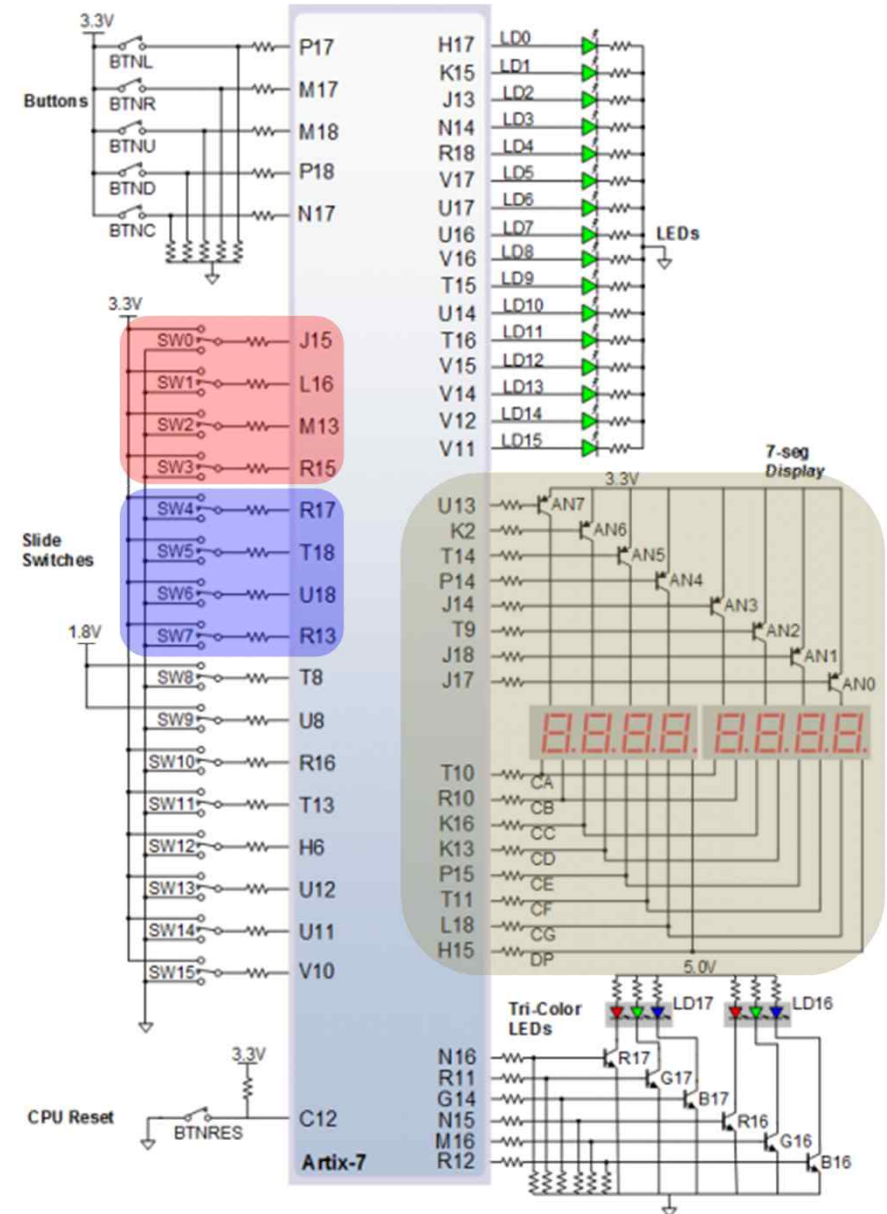 
# FPGA Board 소개

- Digilent Nexys A7 board
  - ✓ FPGA chip: Xilinx Artix-7




# 실험

## • 1) Top 모듈 설계 (LabAdd4bit.v)

- ✓ 4bit adder: Binary\_4bit\_Adder.v
- ✓ 7-segment display decoder: Dsp7Seg.v

*LabAdd4bit.v*

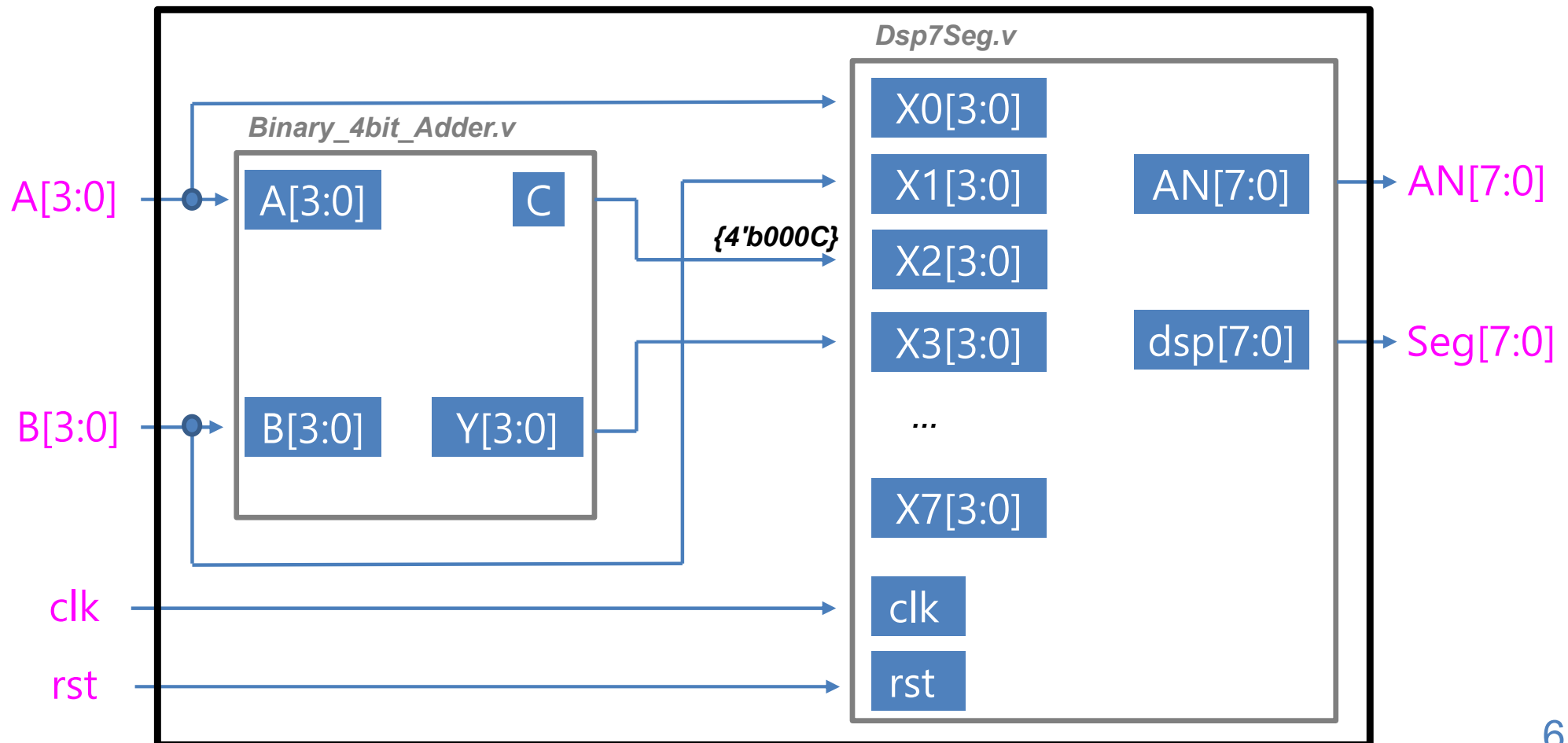

# 실험

- 1) Top 모듈 설계 (LabAdd4bit.v)
  - ✓ 4bit adder: Binary\_4bit\_Adder.v
  - ✓ 7-segment display decoder: Dsp7Seg.v

```
`timescale 1ns / 1ps

module LabAdd4bit( A, B, clk, rst, AN, Seg );

input [3:0] A;
input [3:0] B;
input clk, rst;
output [7:0] AN;
output [7:0] Seg;


wire [3:0] carry, sum;
assign carry[3:1]=3'b000;

Binary_4bit_Adder U1 (.A(A), .B(B), .C(carry[0]), .Y(sum));
Dsp7Seg U2 (.X0(A), .X1(B), .X2(carry), .X3(sum), .clk(clk), .rst(rst), .AN(AN), .dsp(Seg));

endmodule
```
 
## • 2) Pin constraint 작성

- ✓ Constraint 선택 → Add sources
- ✓ Design in/out port를 보드 pin 정보에 맞추어 mapping 필요
  - xdc file 작성
  - <https://github.com/Digilent/digilent-xdc/>





## • 2) Pin constraint 작성


- ✓ Design in/out port를 보드 pin 정보에 맞추어 mapping 필요

D:/1\_work/Xilinx\_work/basic\_circuit\_experiment/basic\_circuit\_experiment.srcs/constrs\_1/new/LabAdd4bit\_const.xdc

```
1
2 set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { clk }]; #IO_L12P_T1_MRCC_35 Sch=clk100mhz
3 set_property -dict { PACKAGE_PIN N17     IOSTANDARD LVCMOS33 } [get_ports { rst }]; #IO_L9P_T1_DQS_14 Sch=btnc
4
5 # input A
6 set_property -dict { PACKAGE_PIN R17     IOSTANDARD LVCMOS33 } [get_ports { A[0] }]; #IO_L12N_T1_MRCC_14 Sch=sw[4]
7 set_property -dict { PACKAGE_PIN T18     IOSTANDARD LVCMOS33 } [get_ports { A[1] }]; #IO_L7N_T1_D10_14 Sch=sw[5]
8 set_property -dict { PACKAGE_PIN U18     IOSTANDARD LVCMOS33 } [get_ports { A[2] }]; #IO_L17N_T2_A13_D29_14 Sch=sw[6]
9 set_property -dict { PACKAGE_PIN R13     IOSTANDARD LVCMOS33 } [get_ports { A[3] }]; #IO_L5N_T0_D07_14 Sch=sw[7]
10
11 # input B
12 set_property -dict { PACKAGE_PIN J15     IOSTANDARD LVCMOS33 } [get_ports { B[0] }]; #IO_L24N_T3_RS0_15 Sch=sw[0]
13 set_property -dict { PACKAGE_PIN L16     IOSTANDARD LVCMOS33 } [get_ports { B[1] }]; #IO_L3N_T0_DQS_EMCCLK_14 Sch=sw[1]
14 set_property -dict { PACKAGE_PIN M13     IOSTANDARD LVCMOS33 } [get_ports { B[2] }]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]
15 set_property -dict { PACKAGE_PIN R15     IOSTANDARD LVCMOS33 } [get_ports { B[3] }]; #IO_L13N_T2_MRCC_14 Sch=sw[3]
16
17 # output AN
18 set_property -dict { PACKAGE_PIN J17     IOSTANDARD LVCMOS33 } [get_ports { AN[0] }]; #IO_L23P_T3_F0E_B_15 Sch=an[0]
19 set_property -dict { PACKAGE_PIN J18     IOSTANDARD LVCMOS33 } [get_ports { AN[1] }]; #IO_L23N_T3_FWE_B_15 Sch=an[1]
20 set_property -dict { PACKAGE_PIN T9      IOSTANDARD LVCMOS33 } [get_ports { AN[2] }]; #IO_L24P_T3_A01_D17_14 Sch=an[2]
21 set_property -dict { PACKAGE_PIN J14     IOSTANDARD LVCMOS33 } [get_ports { AN[3] }]; #IO_L19P_T3_A22_15 Sch=an[3]
22 set_property -dict { PACKAGE_PIN P14     IOSTANDARD LVCMOS33 } [get_ports { AN[4] }]; #IO_L8N_T1_D12_14 Sch=an[4]
23 set_property -dict { PACKAGE_PIN T14     IOSTANDARD LVCMOS33 } [get_ports { AN[5] }]; #IO_L14P_T2_SRCC_14 Sch=an[5]
24 set_property -dict { PACKAGE_PIN K2      IOSTANDARD LVCMOS33 } [get_ports { AN[6] }]; #IO_L23P_T3_35 Sch=an[6]
25 set_property -dict { PACKAGE_PIN U13     IOSTANDARD LVCMOS33 } [get_ports { AN[7] }]; #IO_L23N_T3_A02_D18_14 Sch=an[7]
26
27 # output Seg
28 set_property -dict { PACKAGE_PIN T10     IOSTANDARD LVCMOS33 } [get_ports { Seg[6] }]; #IO_L24N_T3_A00_D16_14 Sch=ca
29 set_property -dict { PACKAGE_PIN R10     IOSTANDARD LVCMOS33 } [get_ports { Seg[5] }]; #IO_25_14 Sch=cb
30 set_property -dict { PACKAGE_PIN K16     IOSTANDARD LVCMOS33 } [get_ports { Seg[4] }]; #IO_25_15 Sch=cc
31 set_property -dict { PACKAGE_PIN K13     IOSTANDARD LVCMOS33 } [get_ports { Seg[3] }]; #IO_L17P_T2_A26_15 Sch=cd
32 set_property -dict { PACKAGE_PIN P15     IOSTANDARD LVCMOS33 } [get_ports { Seg[2] }]; #IO_L13P_T2_MRCC_14 Sch=ce
33 set_property -dict { PACKAGE_PIN T11     IOSTANDARD LVCMOS33 } [get_ports { Seg[1] }]; #IO_L19P_T3_A10_D26_14 Sch=cf
34 set_property -dict { PACKAGE_PIN L18     IOSTANDARD LVCMOS33 } [get_ports { Seg[0] }]; #IO_L4P_T0_D04_14 Sch=cg
35 set_property -dict { PACKAGE_PIN H15     IOSTANDARD LVCMOS33 } [get_ports { Seg[7] }]; #IO_L19N_T3_A21_VREF_15 Sch=dp
```


## • 3) Implementation

✓ Synthesis, please & routing

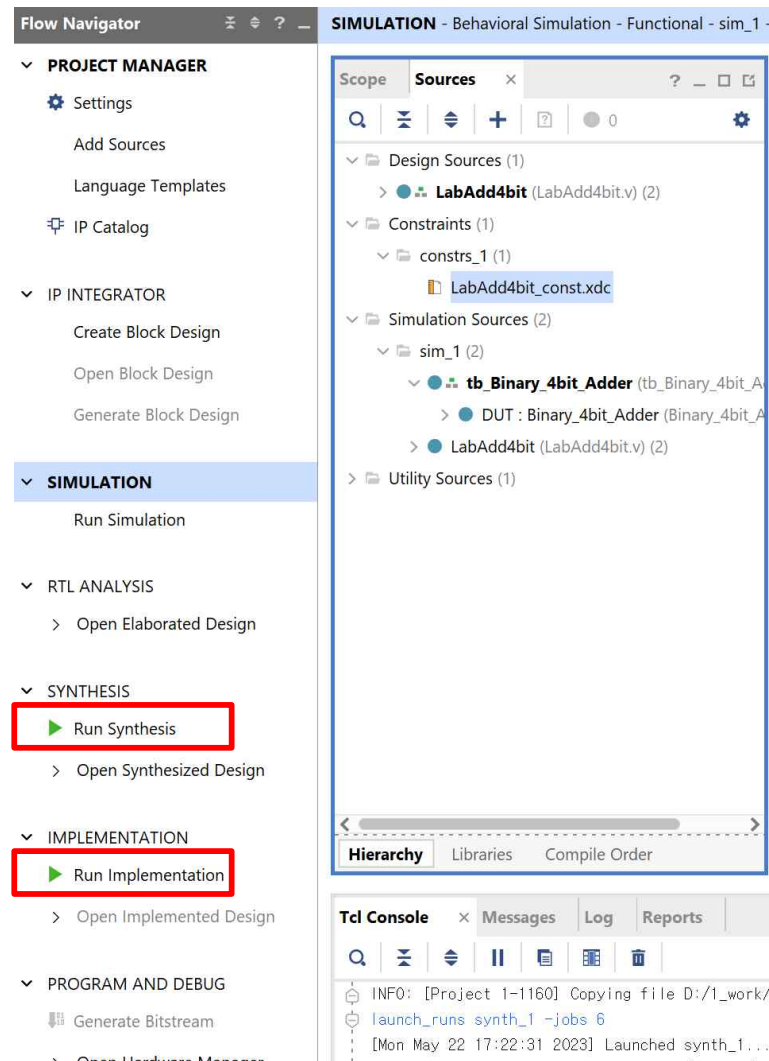

## • 4) Generate Bitstream

- ✓ .bit file generation

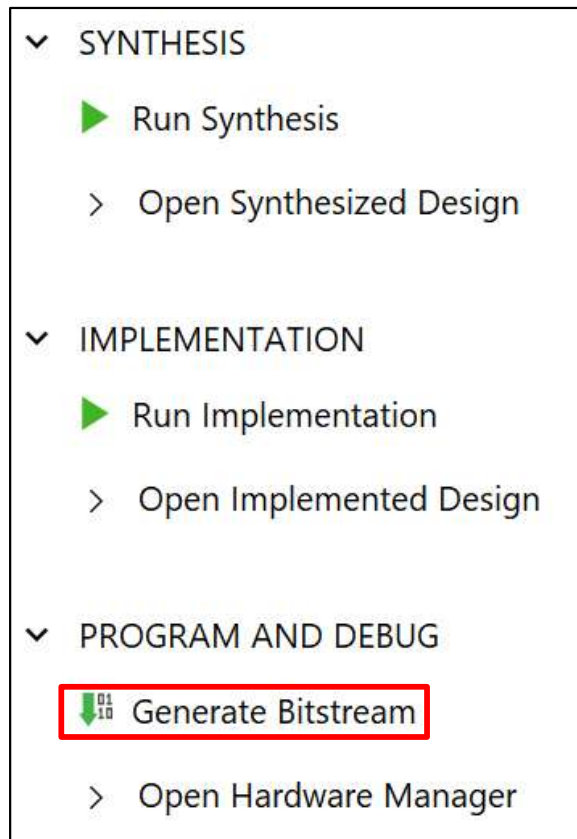

## • 5) Program Device

- ✓ Open Hardware Manager → Open Target
- ✓ Program Device

